

Year 6 Optional Homework Tasks!



Science – Electricity

Science – Electricity

- **Circuit Detective**

Draw and label an electrical circuit with various components (battery, bulb, switch, wires). Explain how the circuit works and what would happen if one part was removed or broken.

- **Electrical Safety Poster**

Create a safety poster for using electricity safely at home or school. Include pictures and short explanations.

